

# ENGR2420: Final Project

## Designing a Rail-to-Rail CMOS Differential Amplifier with a Constant- $g_m$ Rail-to-Rail Input Stage

William Lu

May, 2017

### 1 Simple Rail to Rail Differential Amplifier

With shrinking supply voltages, rail-to-rail differential amplifiers are increasingly important in analog circuit design. To achieve this, the input stage of the differential amplifier can be designed with an N-channel and P-channel differential pair in parallel.

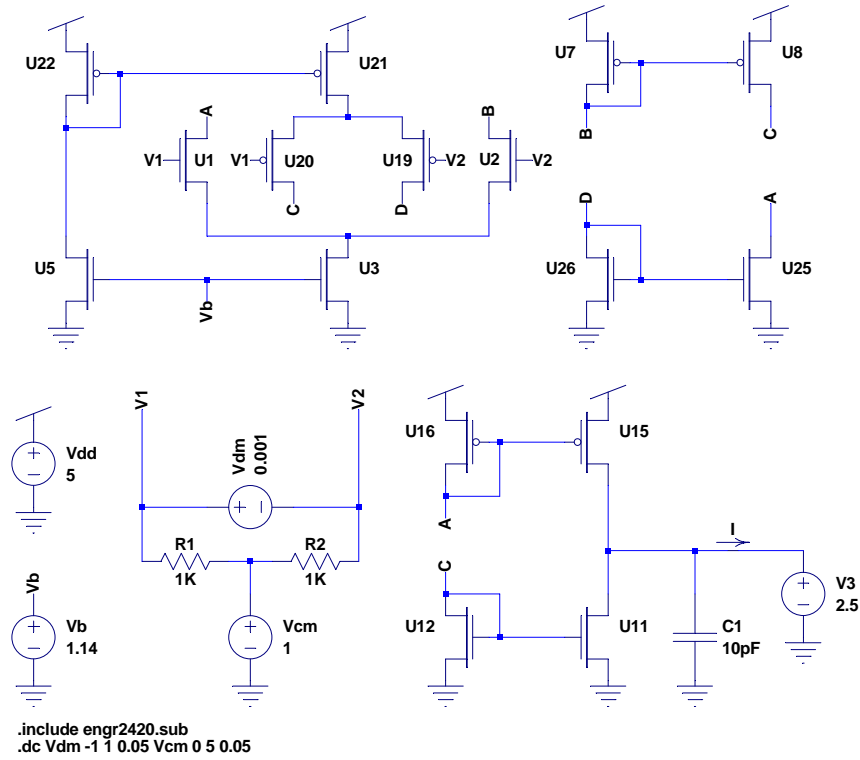


Figure 1: Schematic for a simple rail-to-rail differential amplifier connected as a unity-gain follower with a large load capacitor simulated in LTSpice.

When the common mode voltage ( $V_{cm}$ ) is near the ground rail, only the P-channel differential pair operates, and near the  $V_{DD}$  rail, only the N-channel differential pair operates. However, in between the rails, both differential pairs are operating, which changes the transconductance ( $g_m$ ) of the input stage, making it twice of that when only one differential pair is operating, as shown in Figure 2 on the following page.


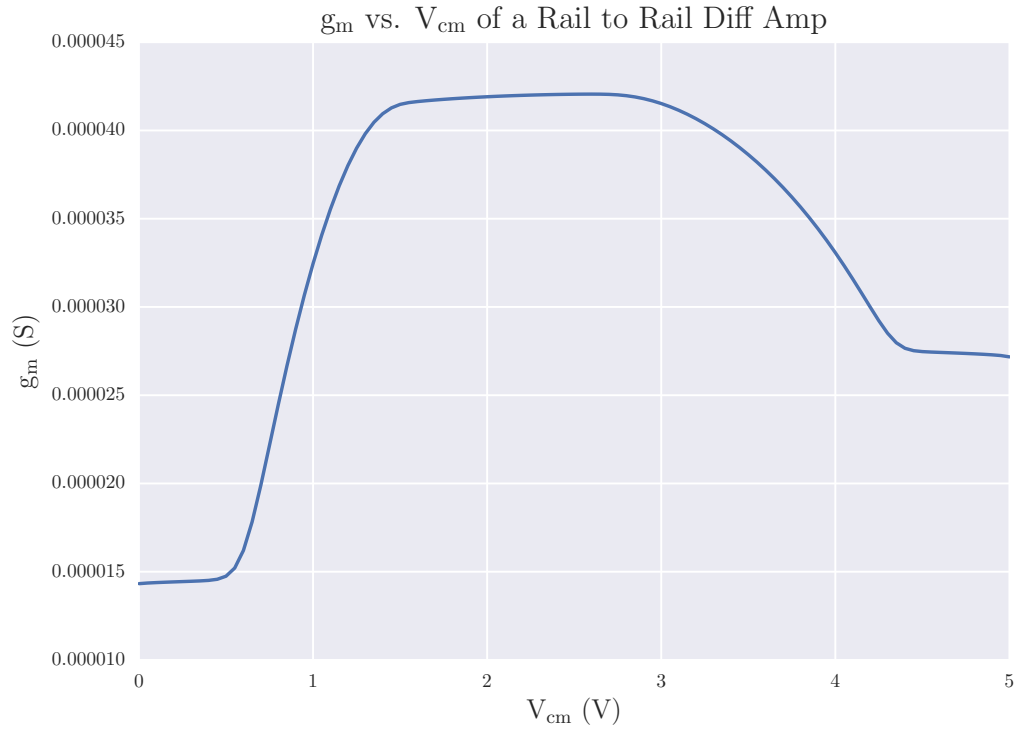


Figure 2: Transconductance of the rail-to-rail differential amplifier shown in Figure 1 on the preceding page versus the common mode voltage ( $V_{cm}$ ).
 
## 2 Constant- $g_m$ Rail to Rail Differential Amplifier

While there are many possible approaches to create a constant- $g_m$  input stage to a rail-to-rail differential amplifier, a simple way to achieve constant- $g_m$  is shown in Figure 3 on the next page.



In the rail-to-rail differential amplifier shown in Figure 1 on page 1, U5 mirrors the bias current ( $I_b$ ) flowing through the nMOS bias transistor, U3, because both U5 and U3 are matched and have the same bias voltage ( $V_b$ ). U22 and U21, which are also matched, form a pMOS current mirror, and because U22 is diode connected, the bias voltage for U21 will cause U21 to have the same  $I_b$  as U3.

Unfortunately, as  $V_{cm}$  leaves the rails, both the N-channel and P-channel differential pairs are active and their transconductances add, as shown in Figure 2 on the previous page. The problem is that the main factor controlling whether or not the N-channel and P-channel differential pairs are active is  $V_{cm}$ .

3

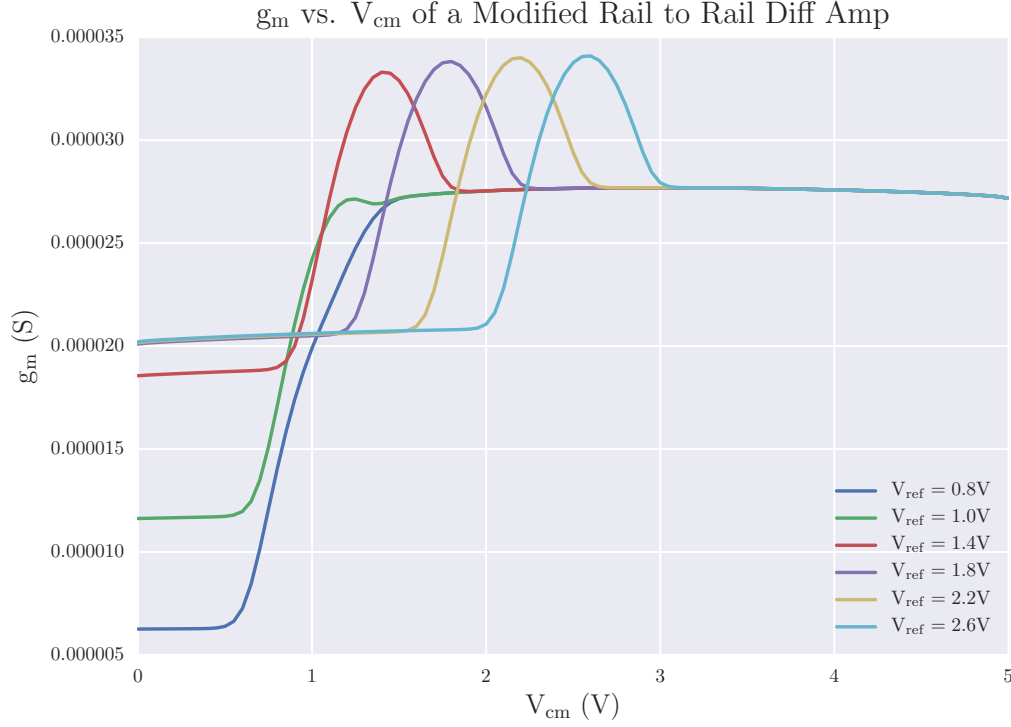


Figure 4: Transconductance of the constant  $g_m$  rail-to-rail differential amplifier shown in Figure 3 on the preceding page versus the common mode voltage ( $V_{cm}$ ).

As  $V_{cm}$  drops from  $V_{DD}$ , the N-channel differential pair will eventually leave saturation. When that happens, current will begin flowing through U34, and the P-channel differential pair will begin to turn on. The current flowing through the P-channel differential pair will experience a proportional increase as the N-channel differential pair drops further and further out of saturation and U3 sources more and more current from U34. The opposite of this process happens when  $V_{cm}$  rises from the ground rail.

As a result, if  $V_{ref}$  is an appropriate value, U34 delays when the initially non-active differential pair turns on, and will only turn on the initially non-active differential pair as the initially active differential pair drops out of saturation. This results in a much flatter  $g_m$  curve from rail to rail, as shown in Figure 4.

When  $V_{cm} = V_{ref}$ , the current flowing through U34, U1, and U2 will all be about  $\frac{1}{3}I_b$ . This is the transition point when one differential pair becomes “more active” than the other differential pair. Because there is still a transition point where both differential pairs are active,  $g_m$  of this circuit is not completely flat, as shown by Figure 4. The peak of the spike in  $g_m$  corresponds to  $V_{ref}$  and where both differential amplifiers are contributing most to the overall transconductance of the circuit. It is, however, possible to tune  $V_{ref}$  to reduce or eliminate the spike in  $g_m$  at the cost of some bandwidth. For this simulated circuit, that is at about 1.04V.

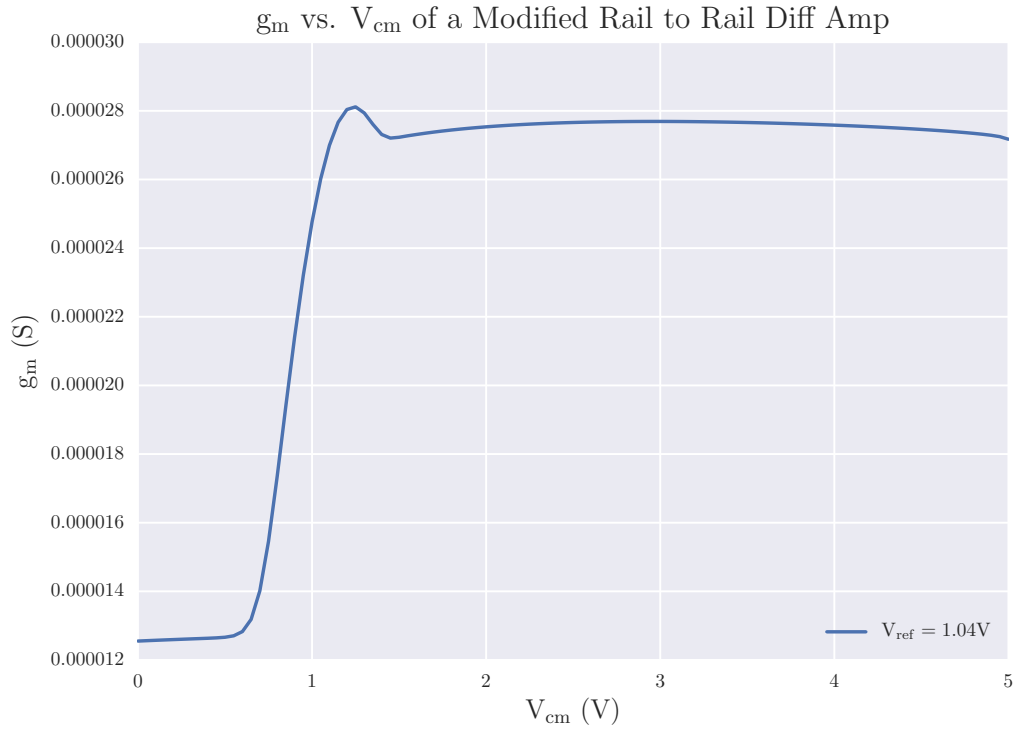


Figure 5: Transconductance of the constant  $g_m$  rail-to-rail differential amplifier shown in Figure 3 on page 3 versus the common mode voltage ( $V_{cm}$ ) when  $V_{ref}$  is set to 1.04 V.

Another reason why the  $g_m$  characteristic for this circuit is not completely flat is due to electron/-hole mobility in nMOS and pMOS transistors. Because holes are less mobile than electrons, the pMOS transistors in this simulated circuit have a smaller transconductance gain than the nMOS transistors. This is why the  $g_m$  drops as  $V_{cm}$  approaches ground.

## 2.1 Below Threshold

When the bias transistor is below threshold, the spike in  $g_m$  is much smaller, as shown in Figure 6 on the next page.

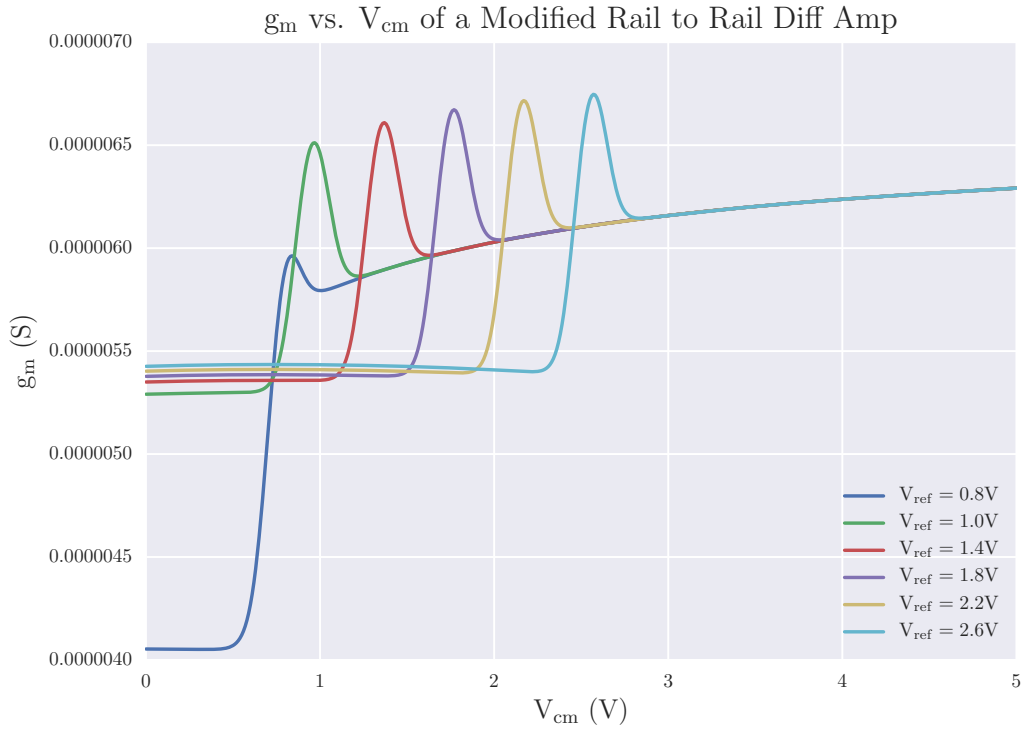


Figure 6: Transconductance of the constant  $g_m$  rail-to-rail differential amplifier shown in Figure 3 on page 3 versus the common mode voltage ( $V_{cm}$ ) when the bias transistor is below threshold.

### 3 Appendix

To access the spice files and code for this project, go to my GitHub repository: <https://github.com/williamalu/CircuitsProject>

### References

- [1] Lu, Yan and Yao, Ruo He *Low-voltage constant- $g_m$  rail-to-rail CMOS operational amplifier input stage*. Solid State Electronics, Elsevier, 2008.
- [2] Minch, Bradley A. *A Low-Voltage MOS Cascode Bias Circuit For All Input Levels*. Cornell University, 2002.